

Topic 6



Latches and Flip Flops

Introduction

- Beginning from this lecture, we will:
 - Design a new type of building blocks, **latch & flip-flop**, that store value of a bit, a sequential circuit
 - Combine the blocks to build multi-bit storage – a **register**
 - Describe the sequential behavior of a digital circuit using a **finite state machine (FSM)**
 - Convert a finite state machine to a **controller** – a sequential circuit having a register and combinational logic

Reality of Combinational Circuit


Non-Ideal Gate Behavior -- Delay

  

- Real gates have some delay
 - Outputs don't change immediately after inputs change

 
Example of Needing Bit Storage

- Flight attendant call button
 - Button pressed: provides a “1”
 - Press call: light turns on
 - **Stays on** after button released
 - Press cancel: light turns off
 - Logic gate circuit to implement this?




Doesn't work. $Q=1$ when $\text{Call}=1$, but doesn't stay 1 when Call returns to 0

 
Need some form of “storage” in the circuit



1. Call button pressed – light turns on

 



2. Call button released – light stays on

 

  3. Cancel button pressed – light turns off

First Attempt at Implementation of Bit Storage


- We need some sort of feedback
 - Does circuit on the right do what we want?
 - Partially: Once Q becomes 1 (when S=1), Q stays 1 forever – no value of S can bring Q back to 0



Concepts of Sequential Circuit

- Sequential circuit

- Combinational circuit with feedbacks

 

- Due to the feedback, output of a sequential circuit is decided by
 - Present inputs, and
 - Past input sequence and
 - Past outputs sequence








- Timing concepts

- input-output propagation delay
- clock
- Other timing issues

Second Attempt at Bit Storage – SR Latch



- Cross-coupled NOR gates
 - S: set (or preset) to 1
 - R: reset (or clear) to 0

Recall...

       

  
Example Using SR Latch for Bit Storage

- SR latch can serve as a bit storage, for example:
 - Call=1 : sets Q to 1
 - Q stays 1 even after Call=0
 - Cancel=1 : resets Q to 0
- But, there's a problem...




Problem with SR Latch

 - Problem
 - If $S=1$ and $R=1$, we don't know what value Q will take when they both return to 0 *simultaneously*



 Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 – but we don't know which.



Representation of SR Latch

- When discussing latches and flip-flops, we use
 - **present state** to represent current value of the Q output
 - **next state** to represent the new value of Q output responding to the current inputs and feedback of current output
- Characteristic table

S(t)	R(t)	Q(t)	Q(t+Δ) → Q ⁺	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	X	not allowed
1	1	1	X	



		Q ⁺	
		S(t)	
R(t) Q(t)	0	1	
	00	0	1
	01	1	1
	11	0	X
10	0	X	

- Characteristic equation

$$Q^+ = S + R'Q$$

Alternative Implementation of SR Latch

  - The cross-coupled RS latch can be implemented using NAND gates




- Characteristic table

S	R	Q	Q ⁺	
0	0	0	X	not allowed
0	0	1	X	
0	1	0	1	set
0	1	1	1	
1	0	0	0	reset
1	0	1	0	
1	1	0	0	hold
1	1	1	1	


Gated SR Latch

 - SR latch is enabled by a gate control signal G



Characteristic Table

G	S	R	Q ⁺
0	x	x	Q; Latch locked
1	0	0	Q; Hold state
1	0	1	0; Reset state
1	1	0	1; Set state
1	1	1	not allowed

 


Gated SR latch
symbol

Solution to SR Latch Restriction

- Gated D Latch

 
- Solution to the unstable state problem caused by $S = R = 1$ in SR latch



Characteristic Table

G	D	Q ⁺
1	0	0
1	1	1
0	X	Q

 
- The input value is stored into the latch only when gate control G has high level – **Level Sensitive**



D latch
symbol


Gated D Latch – Transparent Latch

 - Properties of the D latch
 - D latch is used as a **temporary storage** for a bit
 - The binary information at the data input of the D latch is **copied** to the Q output when the control input G is high (or enabled)
 - The output Q follows changes on the data input D as long as the control input G is enabled, so called a **transparent** latch



A Typical Control Input – Clock Signal

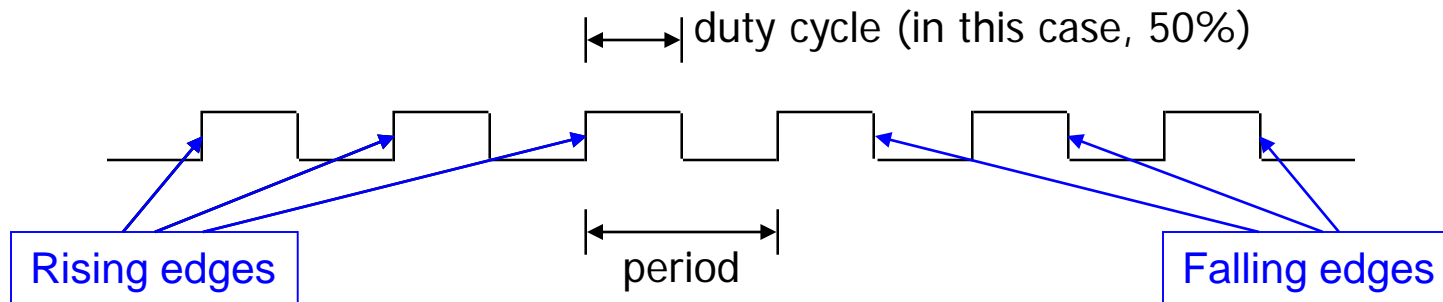
- Periodic pulse train used in sequential circuit to synchronize circuit behaviors



- ***Clock period***: time interval between pulses
- ***Clock cycle***: one such time interval
- ***Clock frequency***: $1/\text{period}$

Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns


Problem with Level-Sensitive D Latch

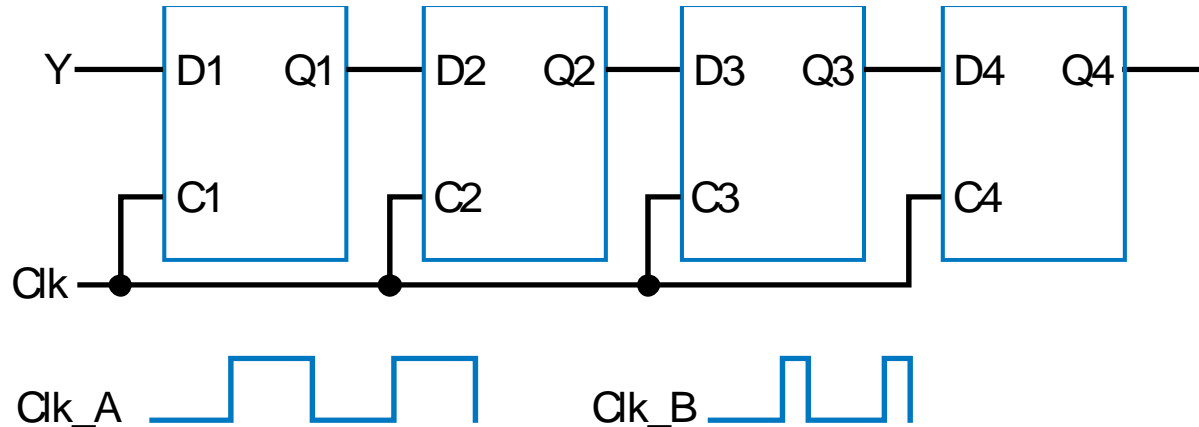


- D latch still has problem
 - When Clk=1, through how many latches will a signal travel?
 - Depends on for how long Clk=1
 - Clk_A -- signal may travel through multiple latches
 - Clk_B -- signal may travel through fewer latches
 - Hard to control the storage elements

Rising-Edge Triggered D Flip Flop

 
- Rising-edge triggered Master-Slave D flip flop



 Alternative Implementation of Rising-Edge Triggered D Flip Flop



Alternative Implementation

 


clock	D	Q ⁺
\uparrow	0	0
\uparrow	1	1
0	X	Q
1	X	Q


Characteristic equation:
 $Q^+ = D$ (at active clock edges)

Rising-Edge Triggered D Flip Flop

 
- Properties of the rising edge triggered D Flip Flop
 - The output changes only at the rising edges of the clock signal – **Edge Sensitive**
 - The output Q gets the value of input D at the time point of rising edge of clock





Symbols for D Flip-Flop

 

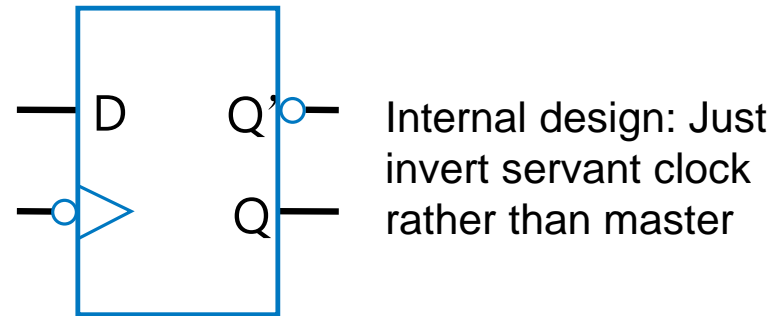Symbol for rising-edge triggered D flip-flop




  Symbol for falling-edge triggered D flip-flop



Application of D Flip-Flop


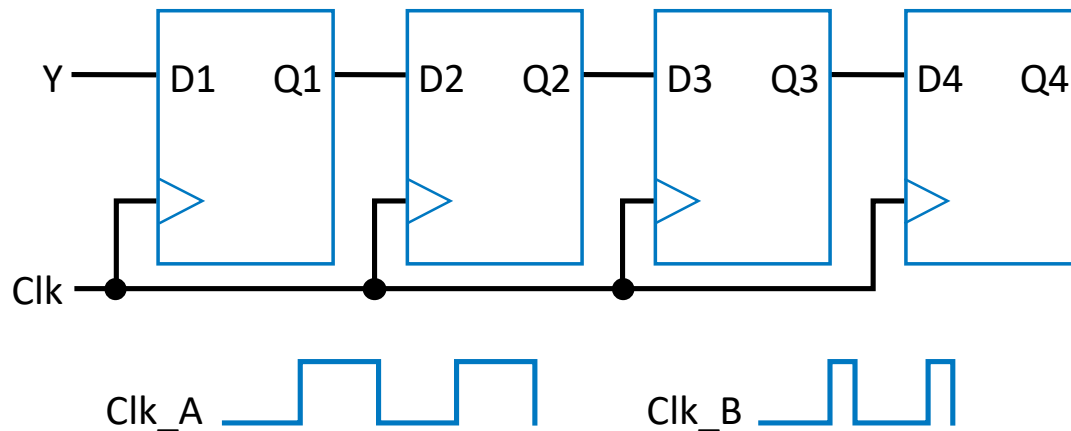
- Solves problem of concatenated D latches when $G=1$
 - In figure below, signal travels through exactly one flip-flop, for either Clk_A or Clk_B
 - On each rising edge of Clk, all four flip-flops are loaded simultaneously, doesn't matter how long Clk is 1.



Flip Flop vs. Latch

- **Both are storage elements in sequential circuits**
- **Flip flop**
 - **edge-sensitive**, the input matters only at active edges (rising or falling)
 - behaviors are **synchronous** to the clock signal
- **Latch**
 - **level-sensitive**, the input matters whenever control has active level (high or low)
 - behaviors are **asynchronous** to the clock signal


Flip Flop vs. Latch

  


Flight-Attendant Call Button Using D Flip-Flop

- D flip-flop will store bit
- Inputs are Call, Cancel, and present output Q of D flip-flop
- Truth table



Call	Cancel	Q	$Q^+ = D$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

 Circuit derived from truth table, using Chapter 2 combinational logic design process






Rising Edge-triggered J-K Flip Flop

  

J	K	Q ⁺
0	0	Q
0	1	0
1	0	1
1	1	Q'


Characteristic equation:
 $Q^+ = JQ' + K'Q$

Rising Edge-triggered T Flip Flop

   



clock	T	Q ⁺
	0	Q
	1	Q'

 Characteristic equation:
 $Q^+ = T'Q + TQ' = T \oplus Q$




Basic Register

  - Typically, we store multi-bit items
 - e.g., storing a 4-bit binary number
- **Register**: multiple flip-flops sharing clock signal




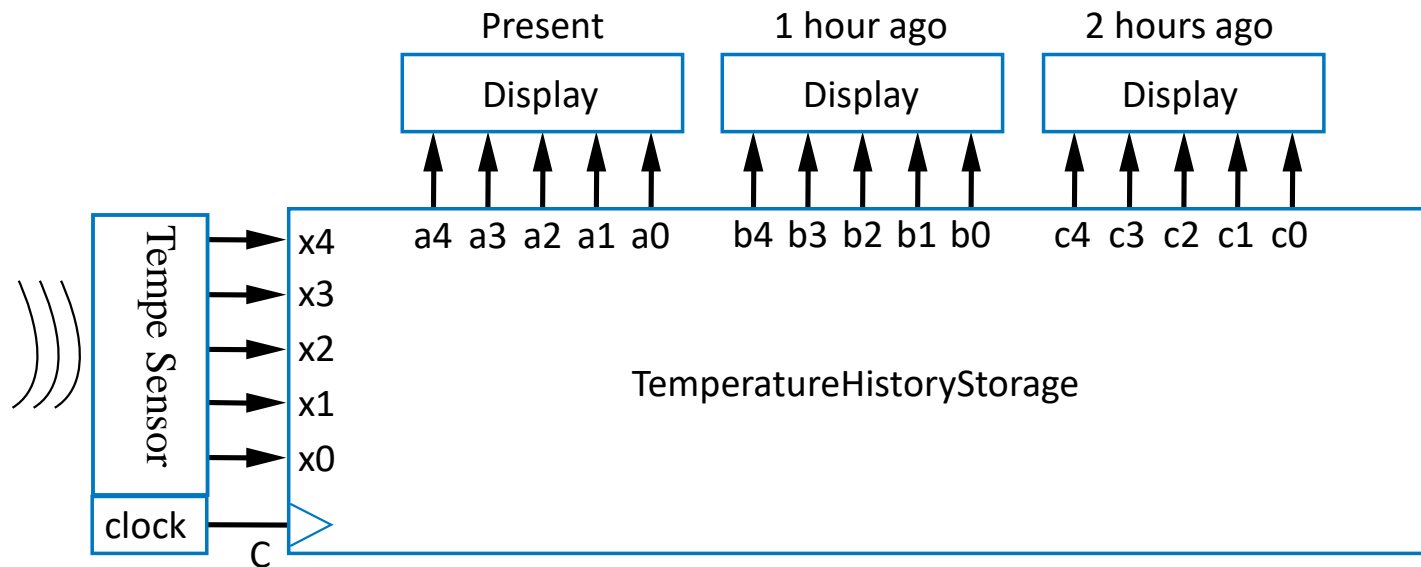
Example Using Registers: Temperature Display

- Temperature history display
 - Sensor outputs temperature as 5-bit binary number
 - Timer pulses C every hour
 - Record temperature on each pulse, display last three recorded values




Example Using Registers: Temperature Display

- Use three 5-bit registers

 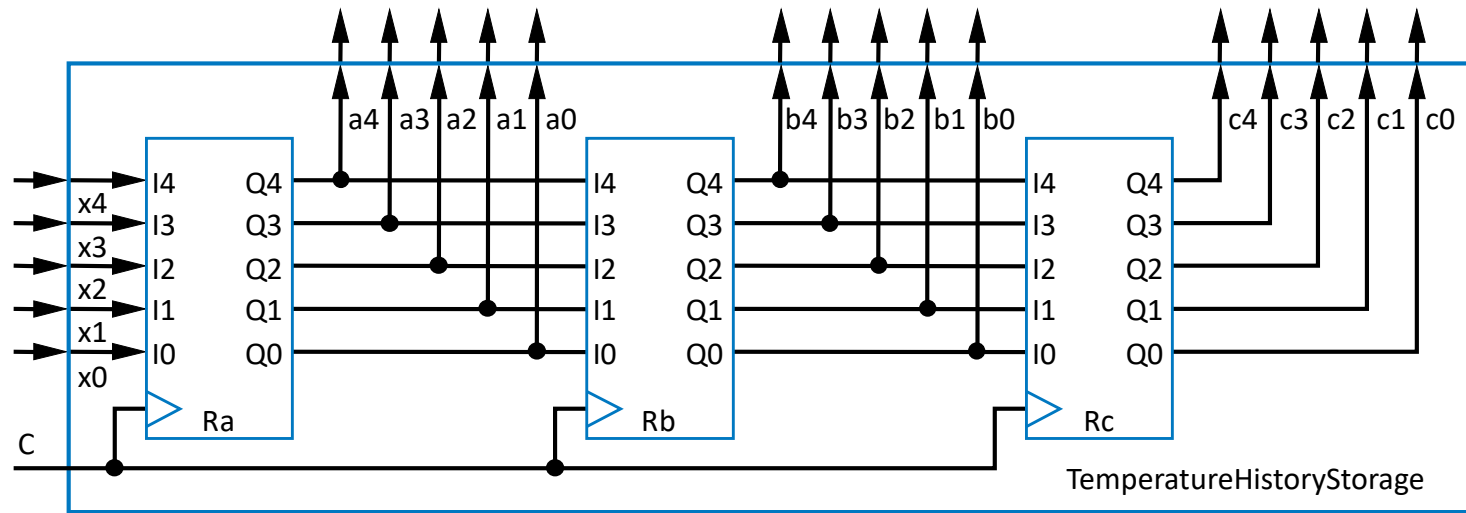


Big Picture – Simplified CPU

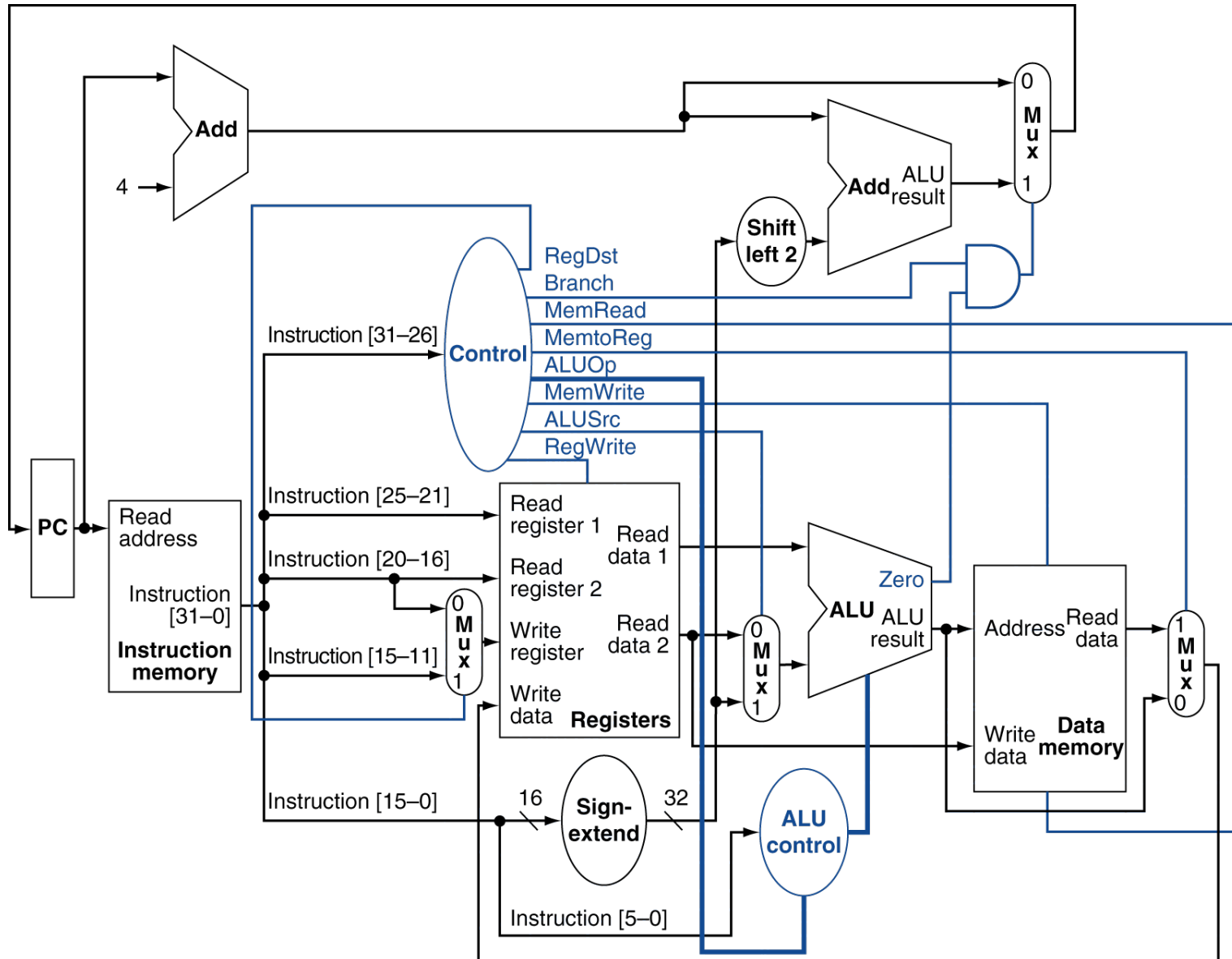


Implementation of Asynchronous Control Input

 Control signals decides the output value directly independent of the clock signal




Control Inputs for Flip Flops

 - Asynchronous:
 - control signals do not depend on the clock signal
- Synchronous:
 - control signals depend on the clock signal
- Active low:
 - It controls when it's low
- Active high:
 - It controls when it's high




Asynchronous Control Input

 - D flip flop with active low asynchronous Clear



Implementation of Synchronous Control Input

 - Synchronous Clear
 - control signal depends on the active edge (either rising or falling) of the clock signal



Flip-Flops with Control Inputs

- D flip flop with active low synchronous Clear

