



**Ve270 Introduction to Logic Design**

**Homework 1**

**Assigned: September 13, 2018**

**Due: September 20, 2018, 4:00pm.**

**The homework should be submitted in hard copies.**

1. Fill out the blank spaces, assuming unsigned numbers. Show steps to earn partial credits. (8 points)

$$1101101.101_2 = \underline{\hspace{2cm}}_{10} = \underline{\hspace{2cm}}_{16}$$

$$78.39_{10} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_8 = \underline{\hspace{2cm}}_3$$

2. Fill out the blank spaces, assuming 2's complement numbers. (16 points)

$$-33_{10} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_{16}$$

$$33_{10} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_{16}$$

$$10110100101_2 = \underline{\hspace{2cm}}_{10}$$

$$F358_{16} = \underline{\hspace{2cm}}_2 = \underline{\hspace{2cm}}_{10}$$

3. Perform the following arithmetic operations step by step, assuming signed numbers: (12 points)

$$(6FE58C + A3DD)_{16} =$$

$$(11100 - 10001111)_2 =$$

$$(532 - 265)_8 =$$

4. Problem 2.14 (Boolean equation = logic equation) (4 points)

2.14 Evaluate the Boolean equation  $F = a \text{ AND } (b \text{ OR } (c \text{ AND } d))$  for the given values of variables  $a$ ,  $b$ ,  $c$ , and  $d$ :

(a)  $a=1, b=1, c=0, d=1$


(b)  $a=0, b=0, c=0, d=1$

(c)  $a=1, b=0, c=0, d=0$

(d)  $a=1, b=0, c=1, d=1$

5. Problem 2.15 (10 points)

2.15 Show the conduction paths and output value of the OR gate transistor circuit in Figure 2.12 when: (a)  $x = 1$  and  $y = 0$ , (b)  $x = 1$  and  $y = 1$ .

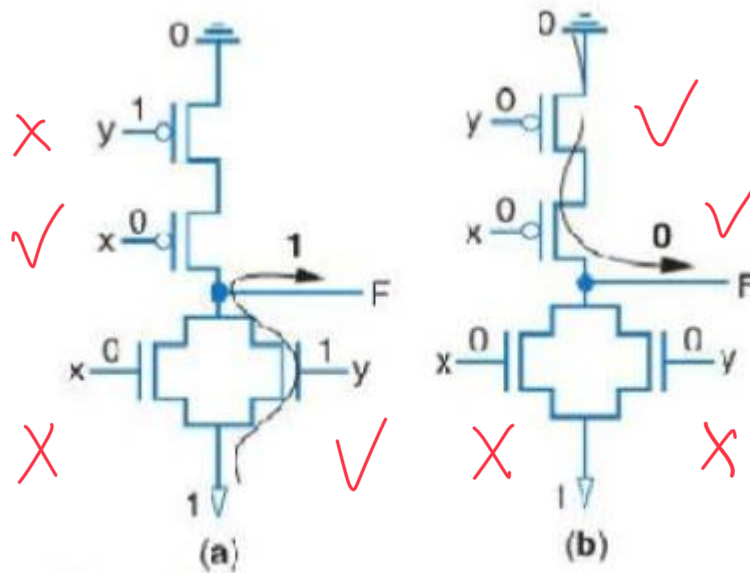

**Figure 2.12** OR gate conduction paths: (a) when one input is 1, and (b) when both inputs are 0.

6. Problem 2.18 (c) (10 points)

**2.18** Convert each of the following equations directly to gate-level circuits:

(a)  $F = a'b' + b'c$

(b)  $F = ab + bc + cd + de$

(c)  $F = ((ab)' + (c)) + (d + ef)'$

7. Problem 2.22 (10 points)

**2.22** Concisely describe the following situation using a Boolean equation. We want to fire a football coach (by setting  $F=1$ ) if he is mean (represented by  $M=1$ ). If he is not mean but has a losing season (represented by the Boolean variable  $L=1$ ), we want to fire him anyway. Write an equation that translates the situation directly to a Boolean equation for  $F$ , without any simplification.

8. Problem 2.35 (c) (d) (10 points)

**2.35** Convert each of the following Boolean equations to a truth table:


(a)  $F(a, b, c) = a' + bc'$

(b)  $F(a, b, c) = (ab)' + ac' + bc$

(c)  $F(a, b, c) = ab + ac + ab'c' + c'$

(d)  $F(a, b, c, d) = a'bc + d'$

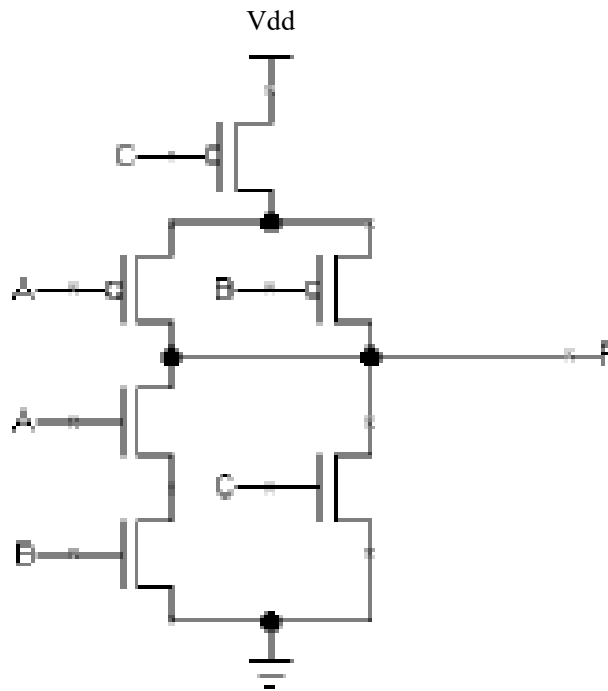9. Build a truth table for the following circuit. (10 points)



10. Given a logic equation  $F = a'c + b'c' + ab$ , draw an output waveform for F based on the given input waveforms. (10 points)

